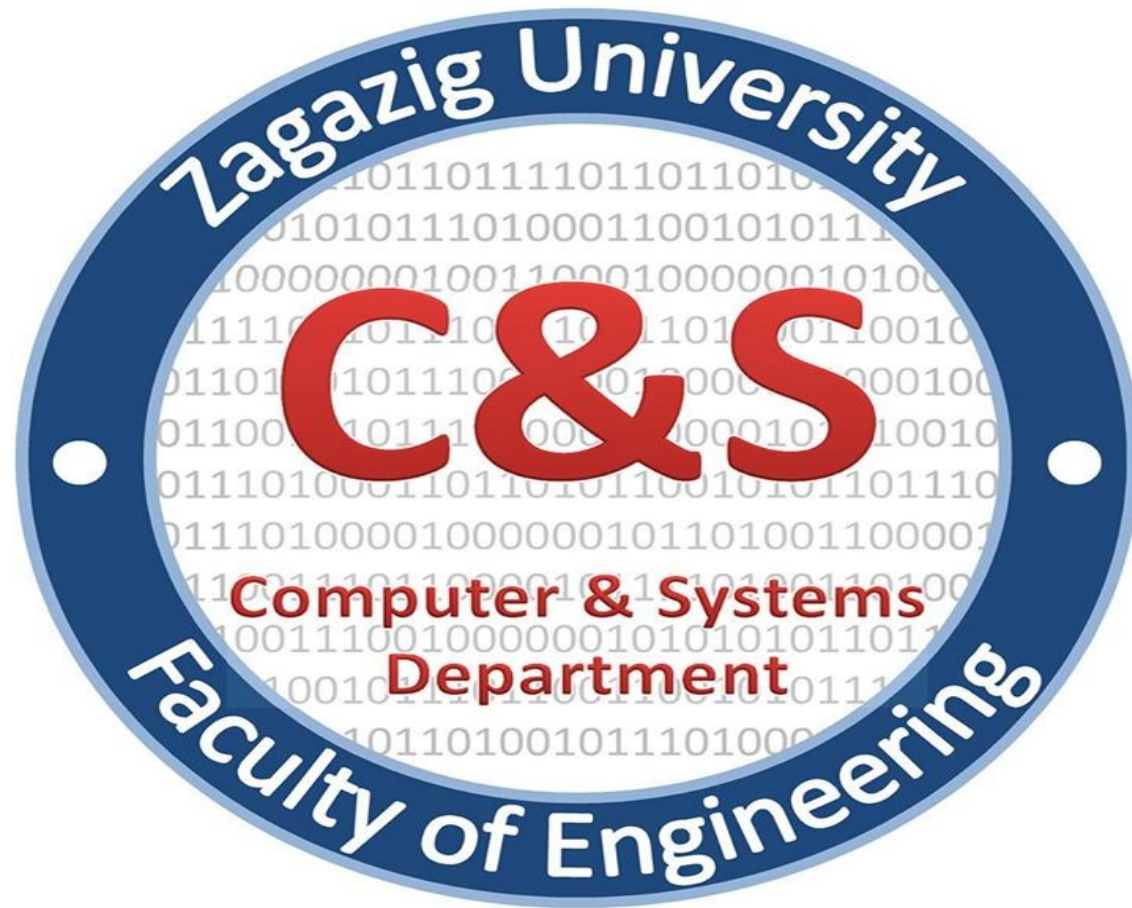


# Temperature control Project



Supervision by :

DR: Ahmed Anany  
[alenany102@gmail.com](mailto:alenany102@gmail.com)

Eng:Hamdy Soltan  
[hamdy.engineer@yahoo.com](mailto:hamdy.engineer@yahoo.com)

# By

1-Ahmed ismail el-sayed

2- Mostafa el-elsayed gohary

3-Eslam mamdouh khalil

4- Aya Ibrahim

5-Ahmed mahmoud ali

6- mahmoud el-sayed hasan

7-mohamed salah Mhamed

# Overflow

We control in the temperature of a room


We set a reference temperature and compare

With the room temperature

If  $T_{\text{room}} > T_{\text{ref}}$  turn on a **fan**

If  $T_{\text{room}} < T_{\text{ref}}$  turn on a **heater**

# Simulation

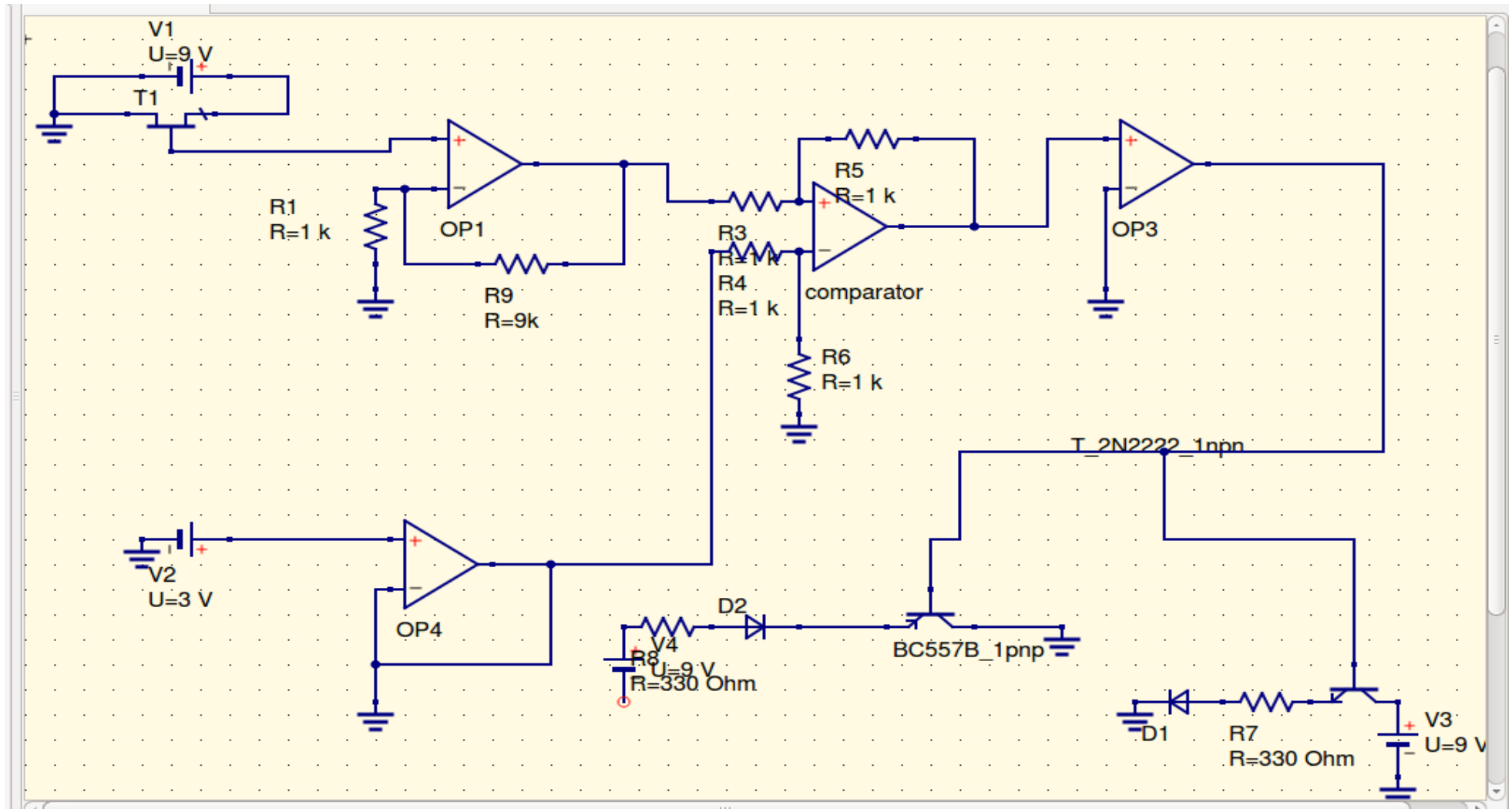

# Component

LM35

4 op-amp 471

Dc -motor

potentiometer


Resisters

Transistor 2n 2222


Transistor Bc557

- LM 35

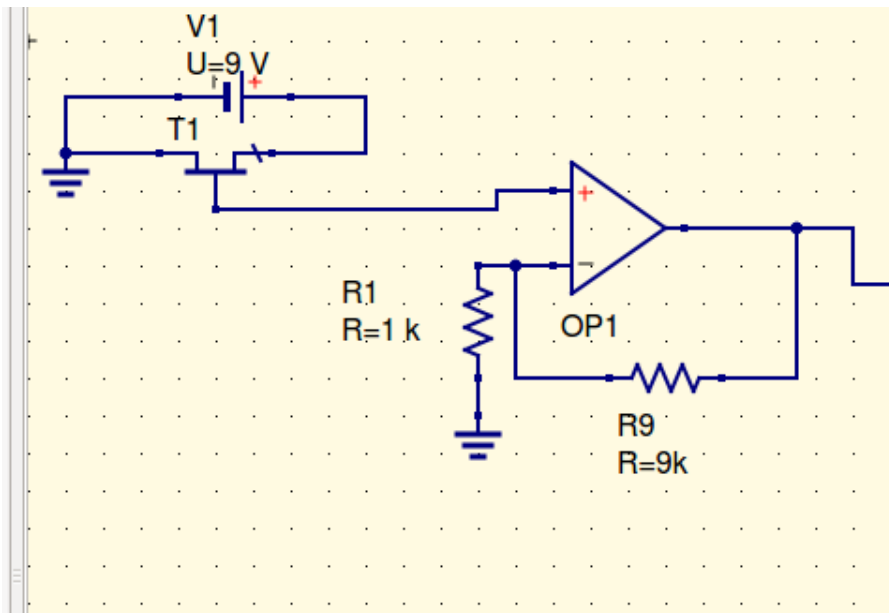
for every one  
temperature the  
sensor out .01 volt  
so we use opAmp  
with gain 10 to  
compare it with the  
reference




- Set the reference Temperature

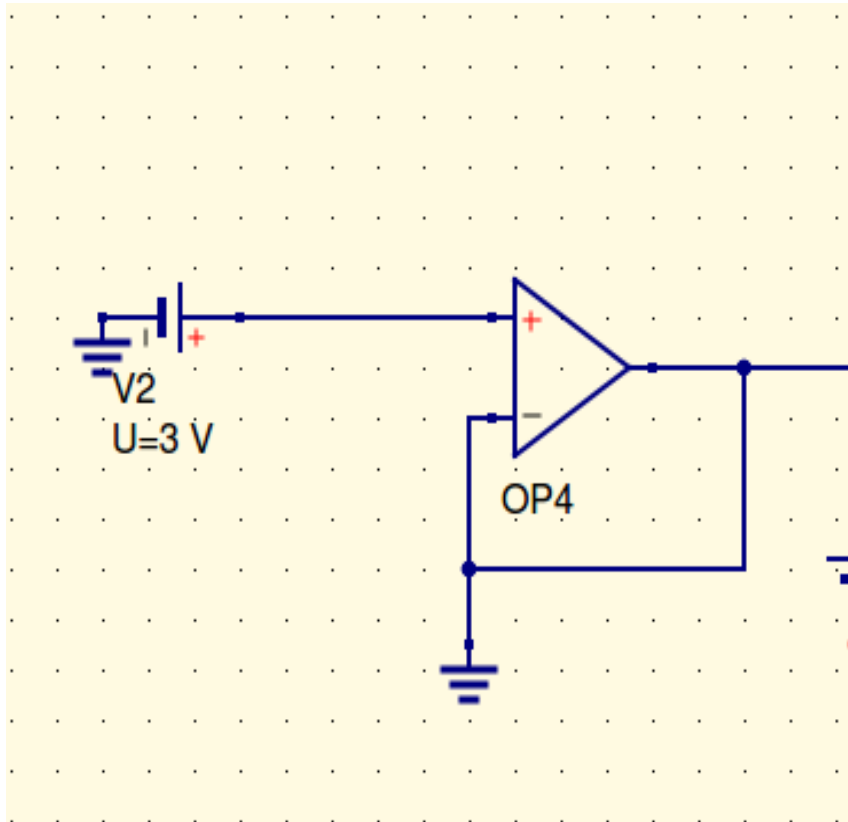




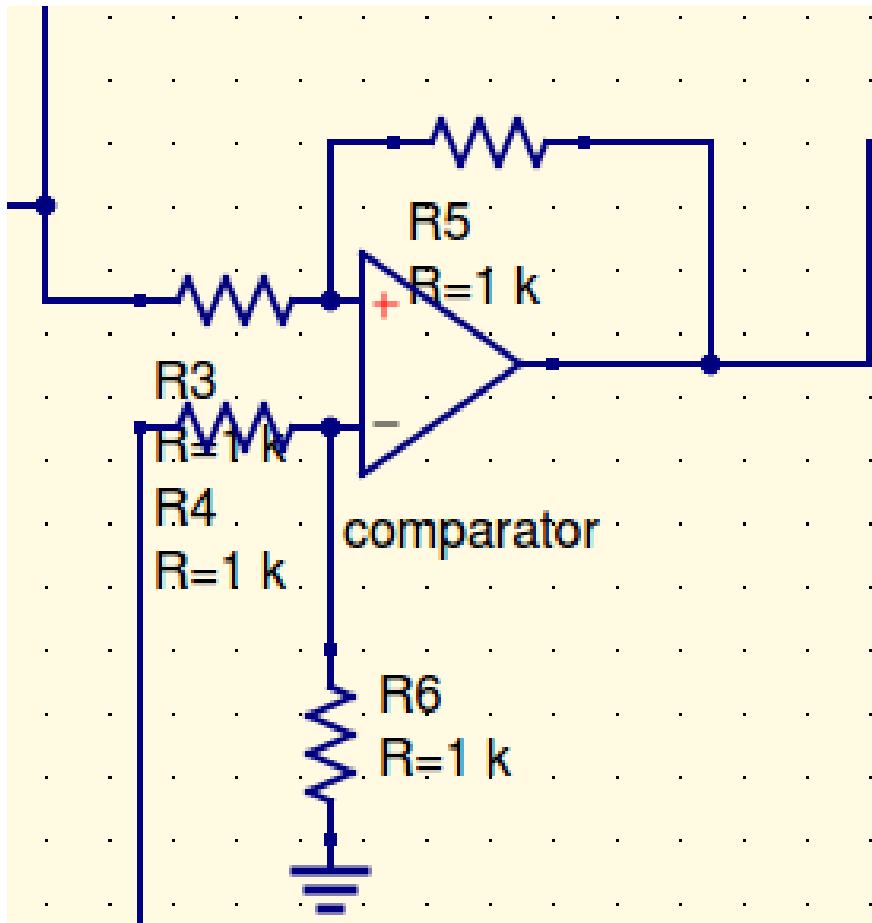

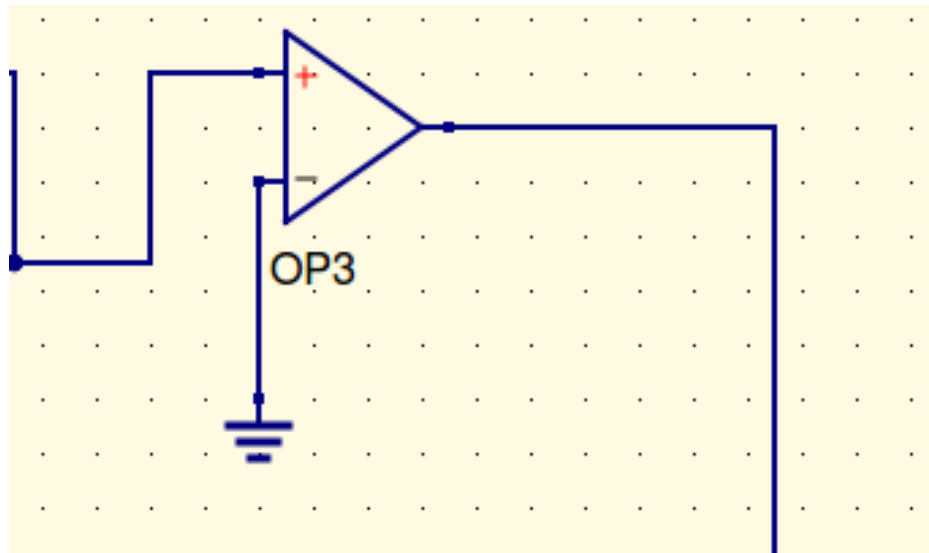- Compare the reference Temperature with the room temperature




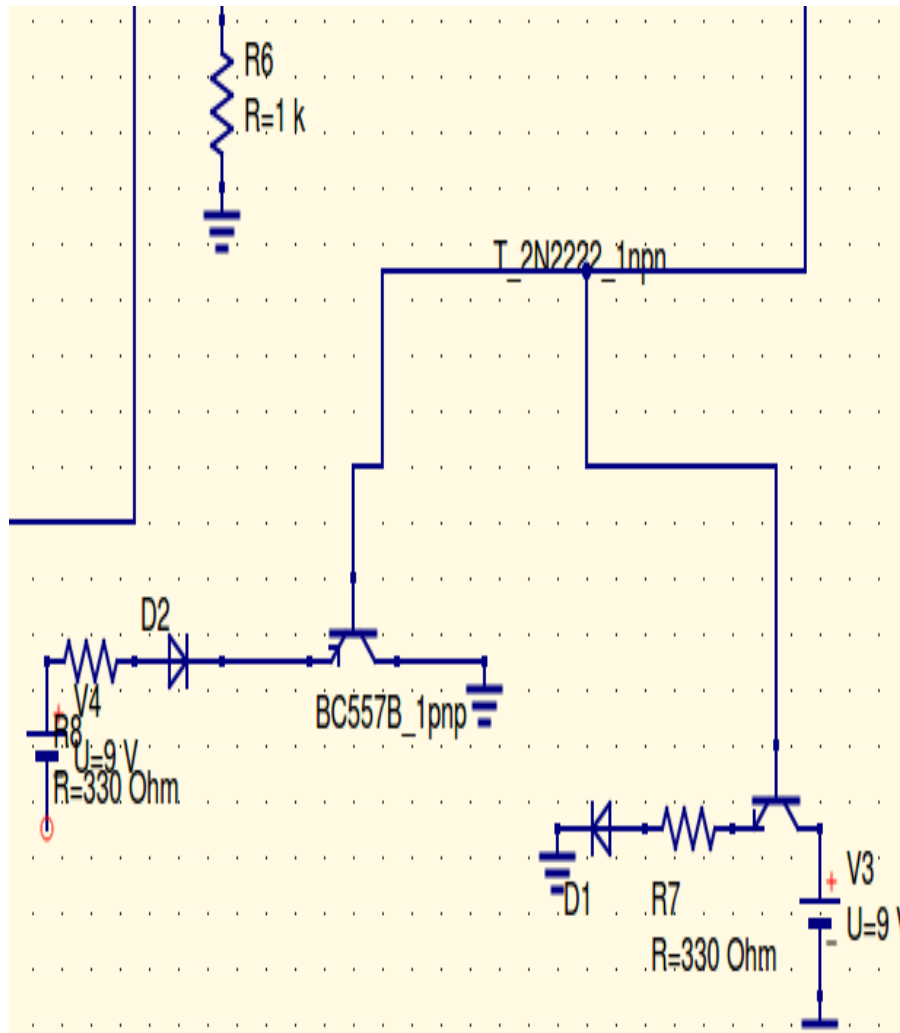- The output voltage is small so we use another comparator **but** with reference **0** and the output become  **$+V_{CC}$  or  $-V_{CC}$**



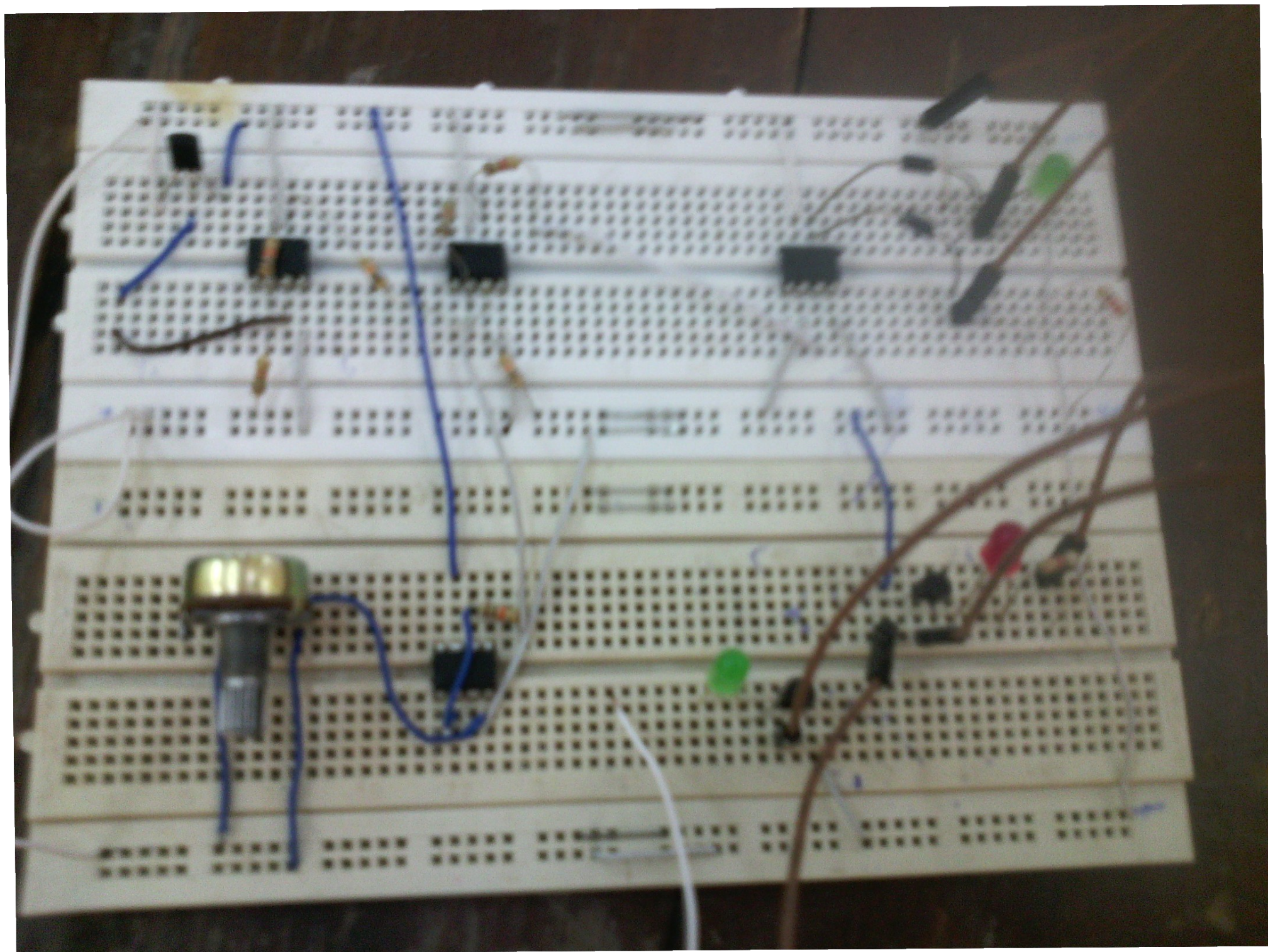
- In case  $+v_{cc}$  the **nnp** transistor work as closed switch and the **fan** work
- In case  $-v_{cc}$  the **pnnp** transistor work as closed switch and the **heater** work







# The fan

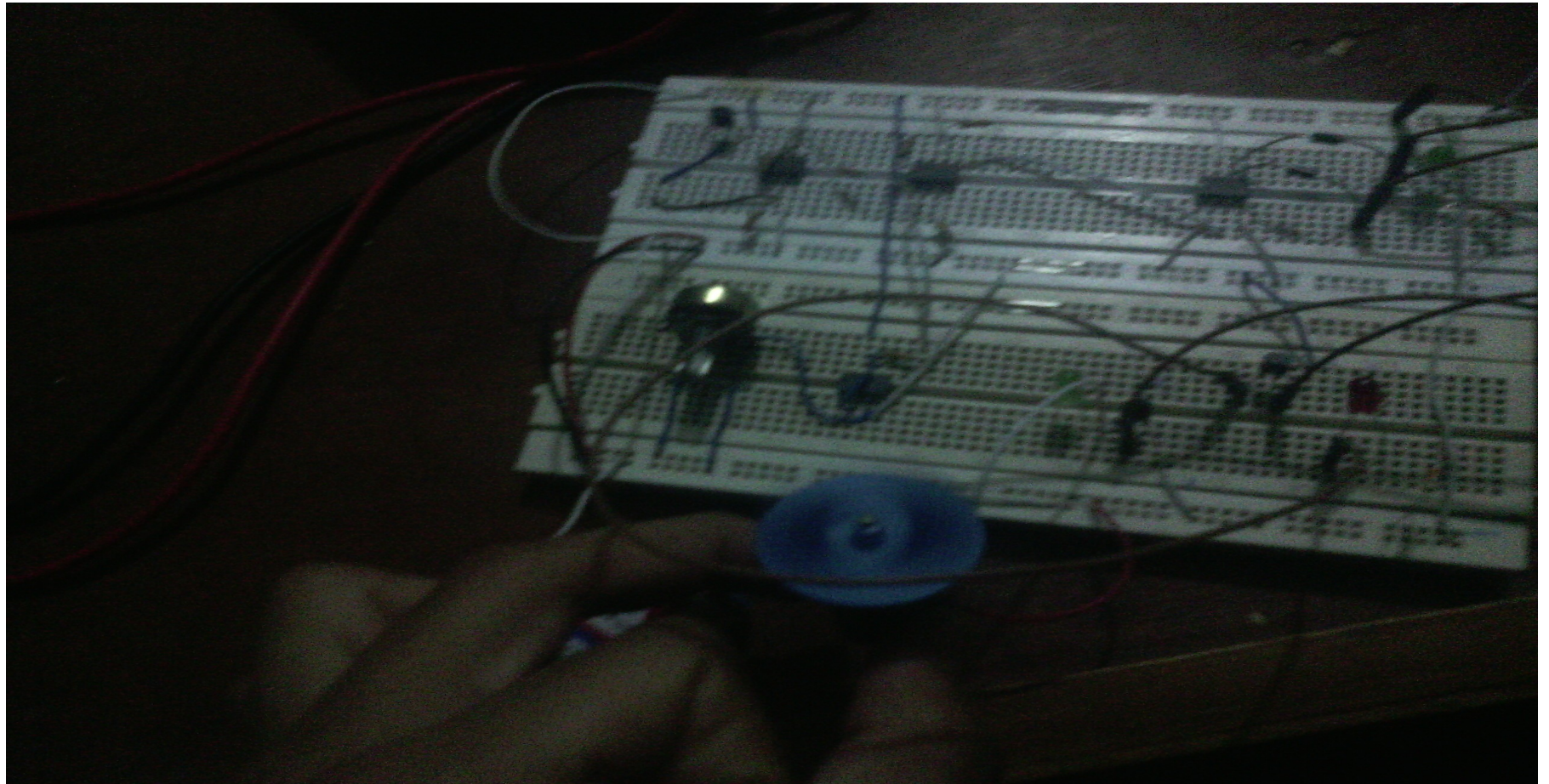

# The heater

